
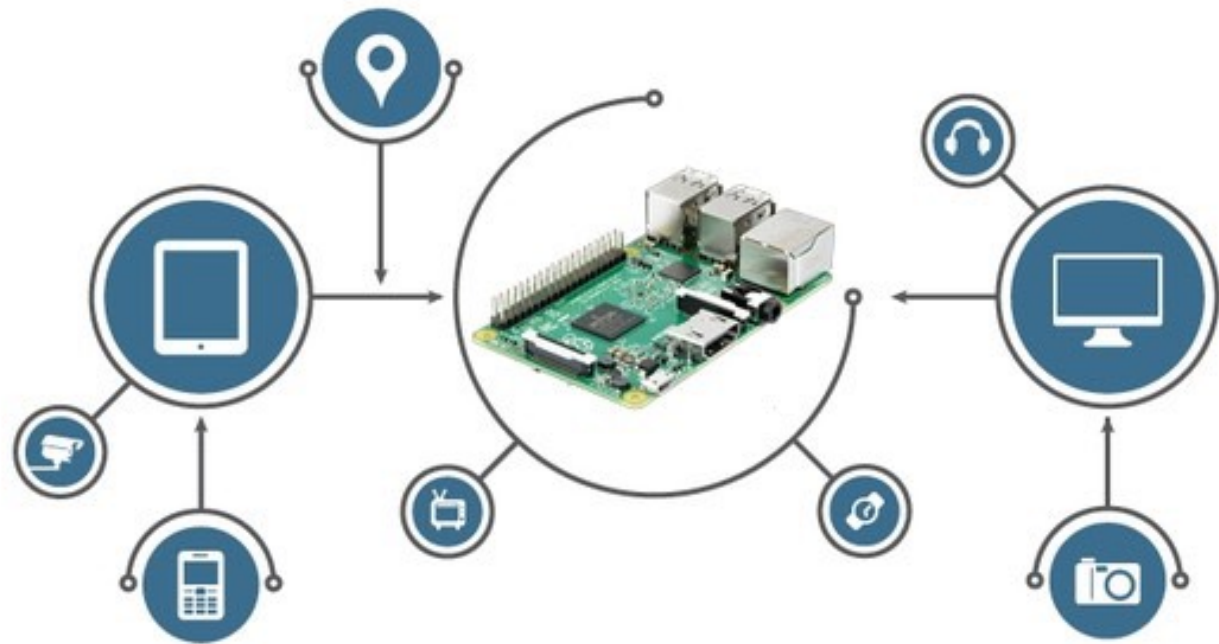


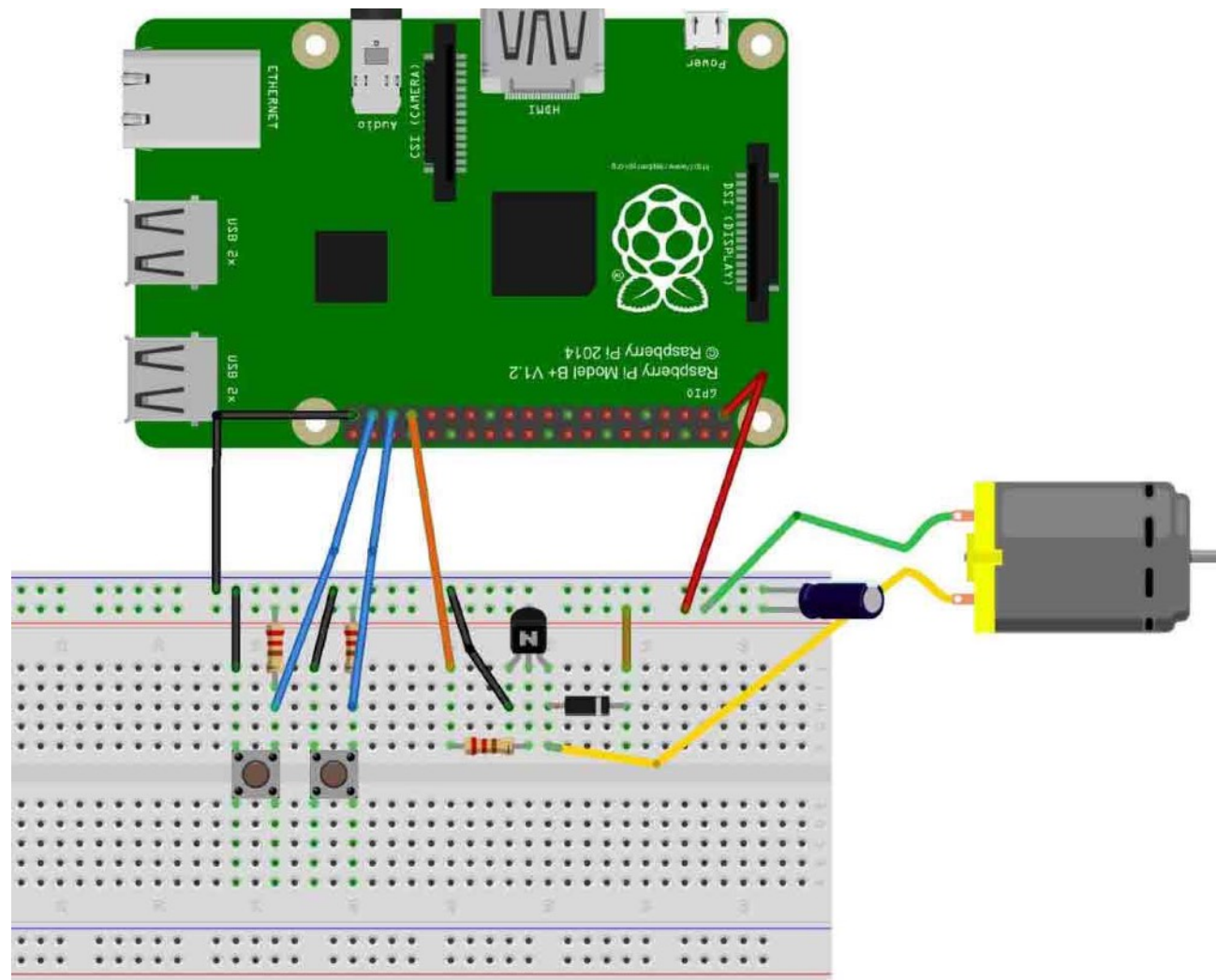


# Raspberry Pi


Working with GPIO Pins



fritzing

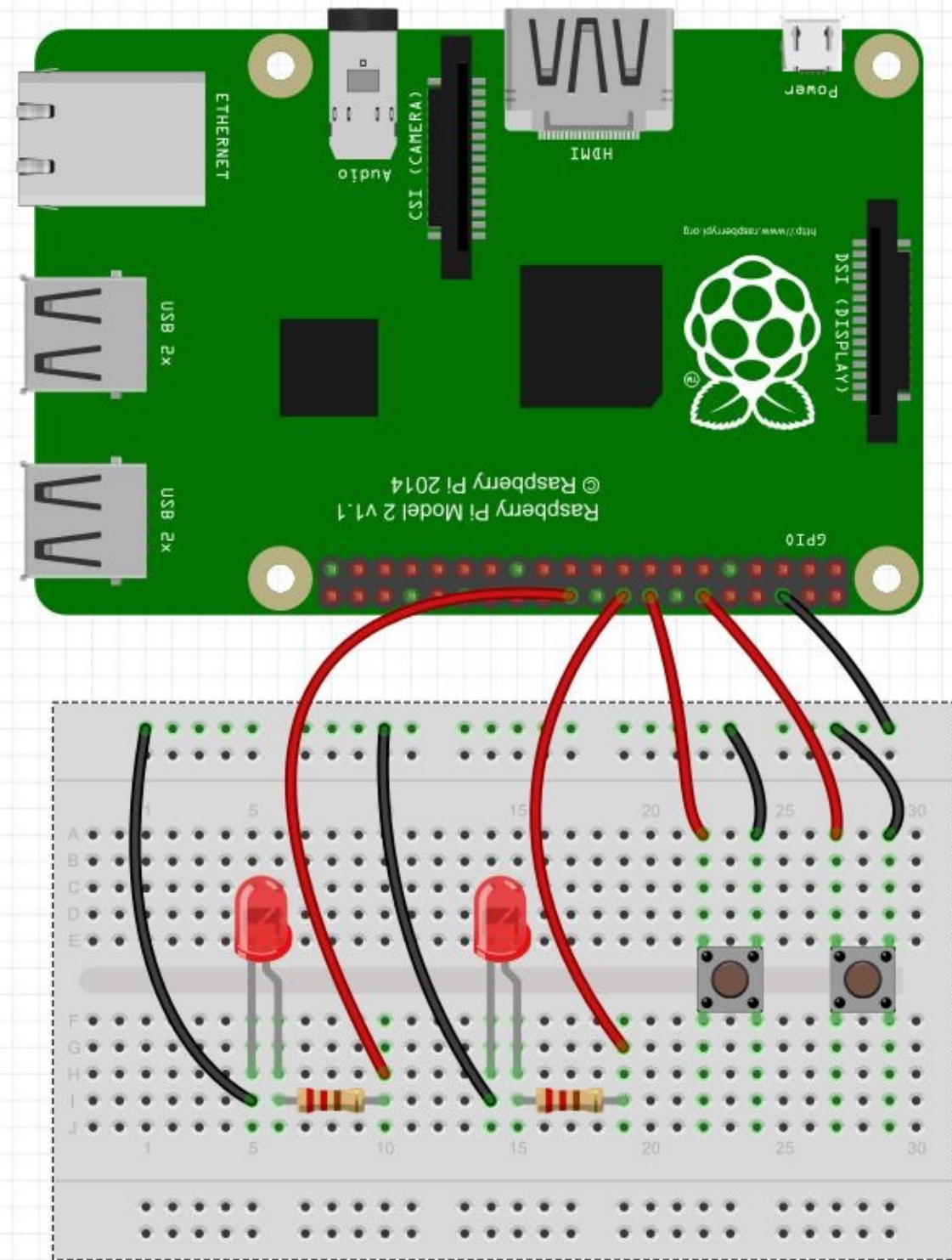



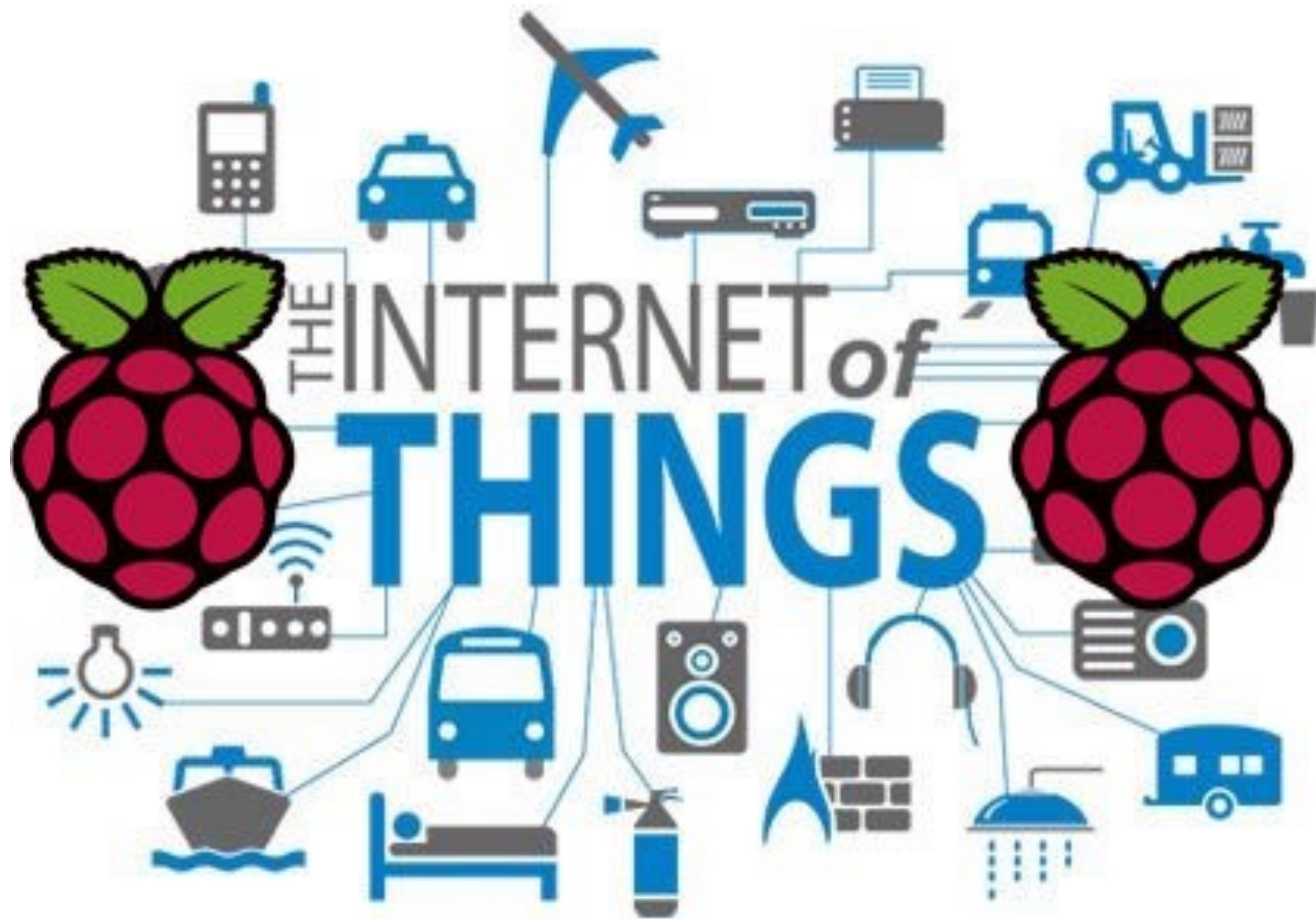






# Tips for reducing the risk of damage to your Raspberry Pi

- Ensure your Pi is powered off when connecting circuitry
- Do not put more than 3.3 V on any GPIO pin
- Do not draw more than 3 mA per output.
- Do not poke at the GPIO connector with a screwdriver or metal object when the Pi is powered on
- Do not power the Pi with more than 5V
- Do not draw more than a total of 50 mA from the 3.3 V supply pins
- Do not draw more than a total of 250 mA from the 5V supply pins






# Raspberry Pi

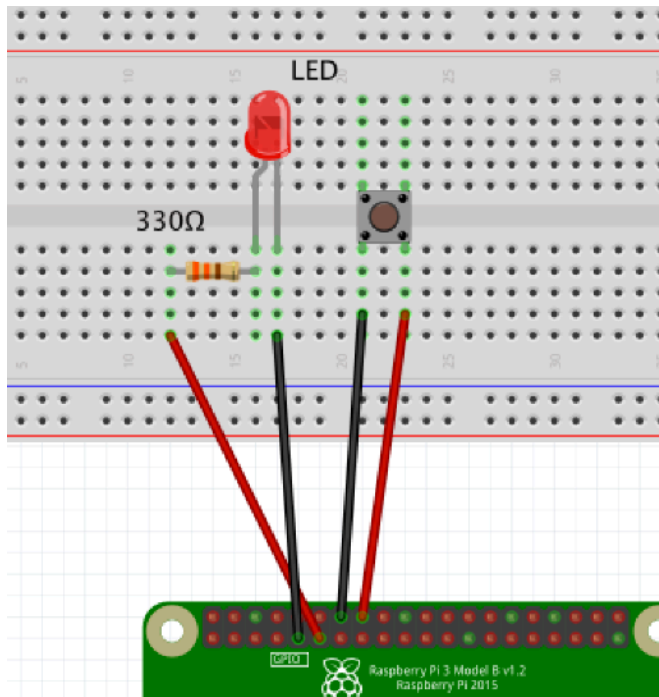

Working with GPIO Pins

Practical Examples

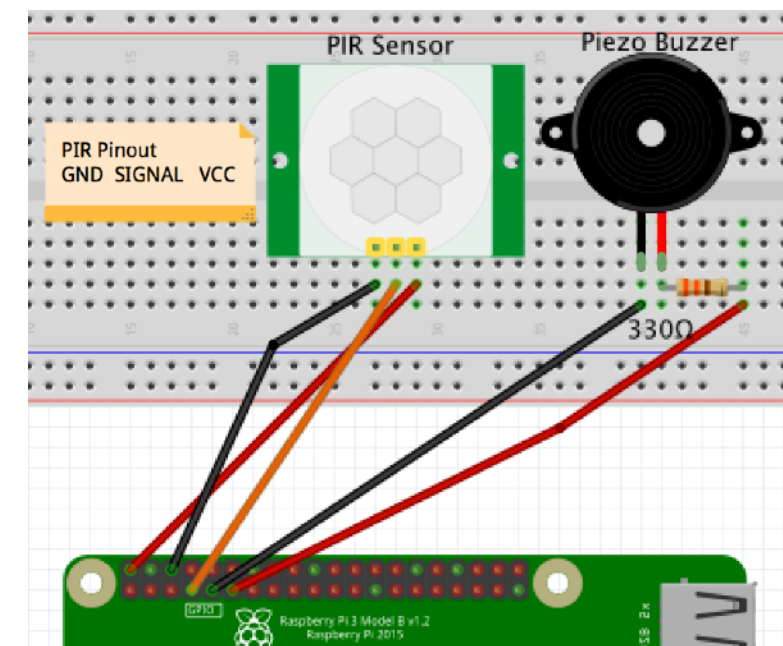

# Standard Raspberry Pi Components needed

- Raspberry Pi 3
- SD Card (flashed with the Raspbian OS)
- USB keyboard
- USB mouse
- Monitor
- HDMI cable
  - Alternative HDMI-VGA adapter if needed
- 5 V Power Supply


# Power an LED

## **Additional parts needed**

- LED
- 330  $\Omega$  resistor
- Connecting wires
  - 2 Male-Female wires



# Power an LED

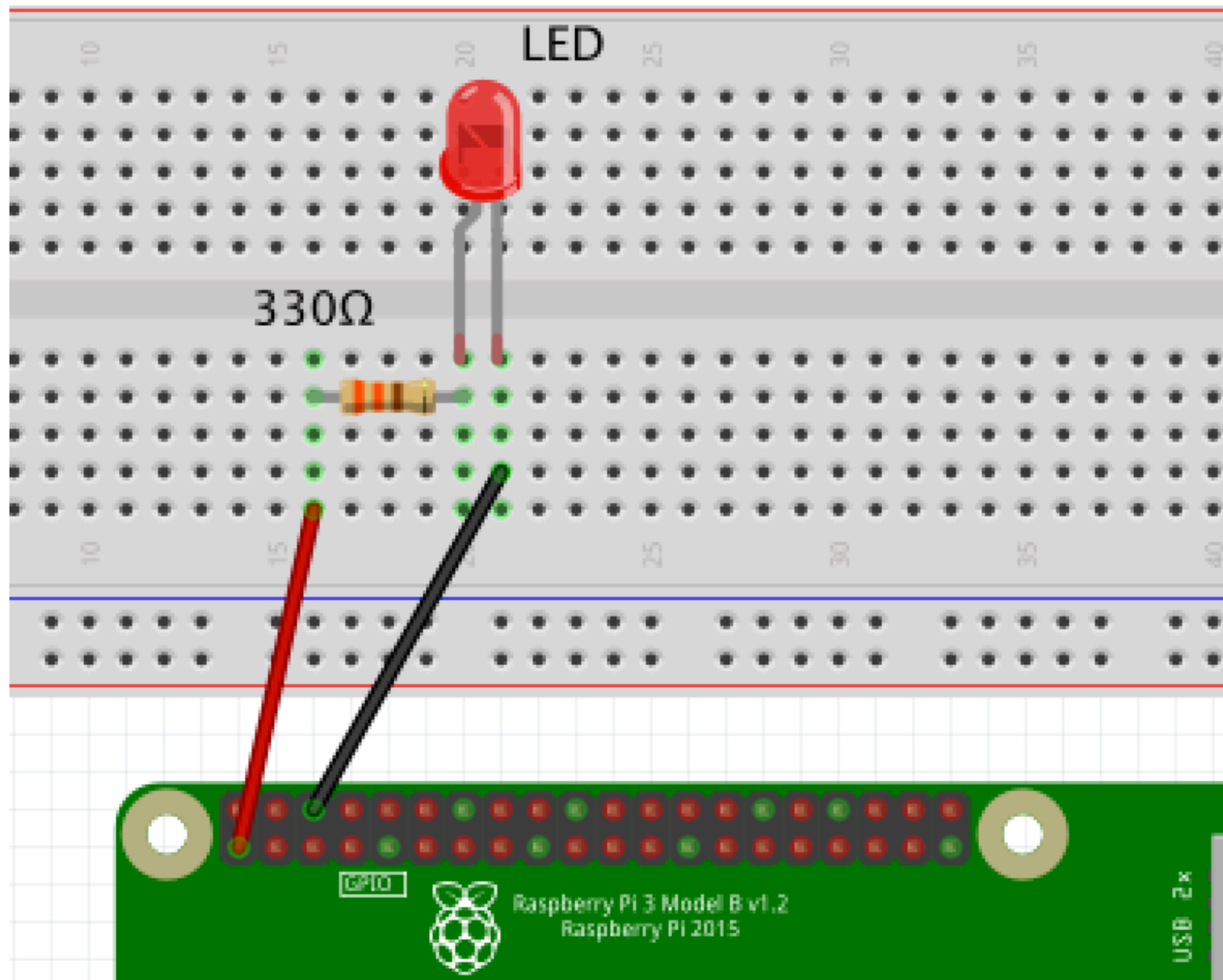


Pin#	GPIO#	Connection
1	3.3V	Resistor to LED Anode
6	GND	LED Cathode

# Blink an LED

## **Additional parts needed**

- LED
- 330  $\Omega$  resistor
- Connecting wires
  - 2 Male-Female wires

# Blink an LED

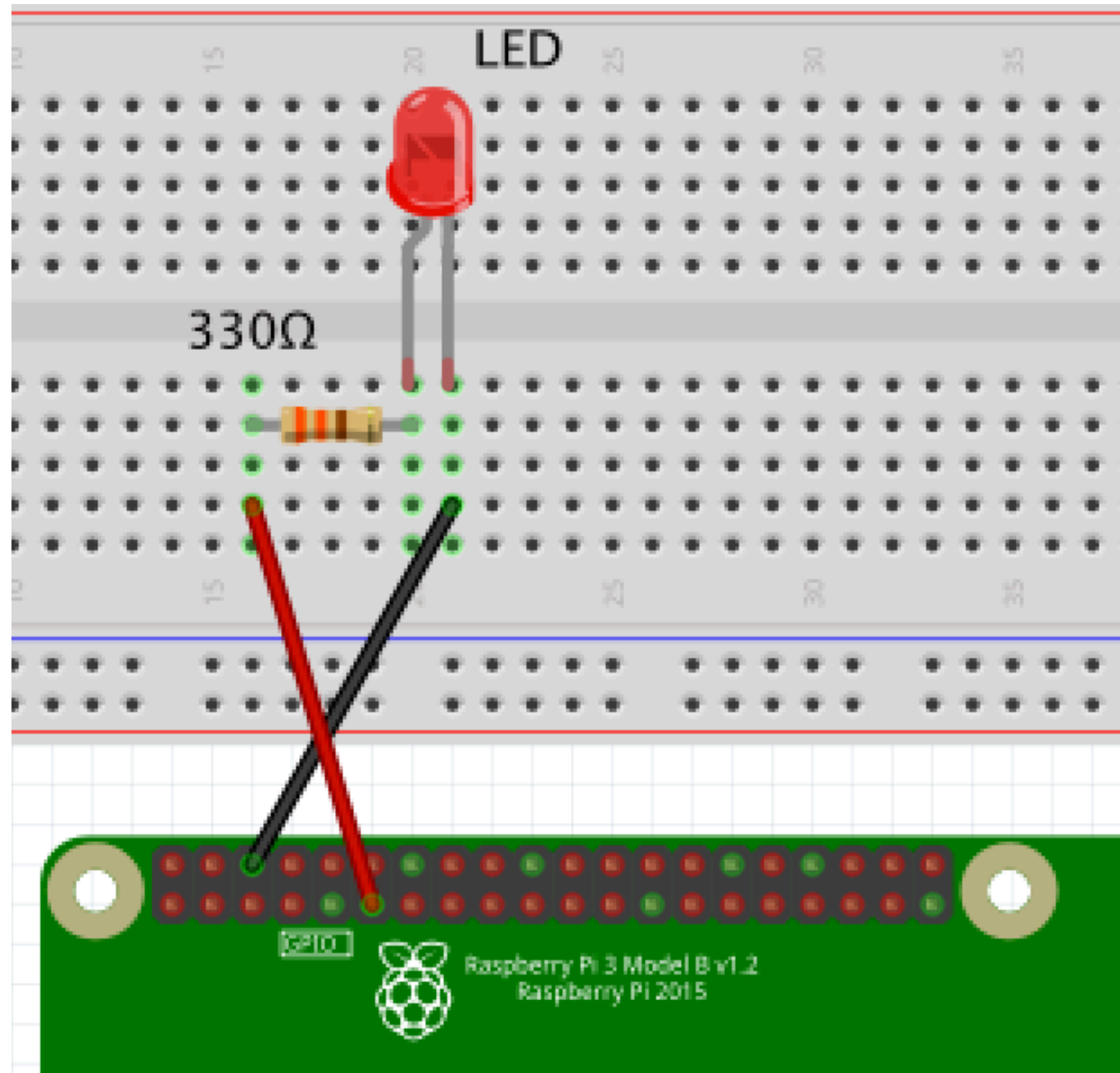

Pin#	GPIO#	Connection
11	GPIO17	Resistor to LED Anode
6	GND	LED Cathode




# Detecting a button press

## **Additional parts needed**

- Push button switch
- Connecting wires
  - 2 Male-Female wires

# Detecting a button press

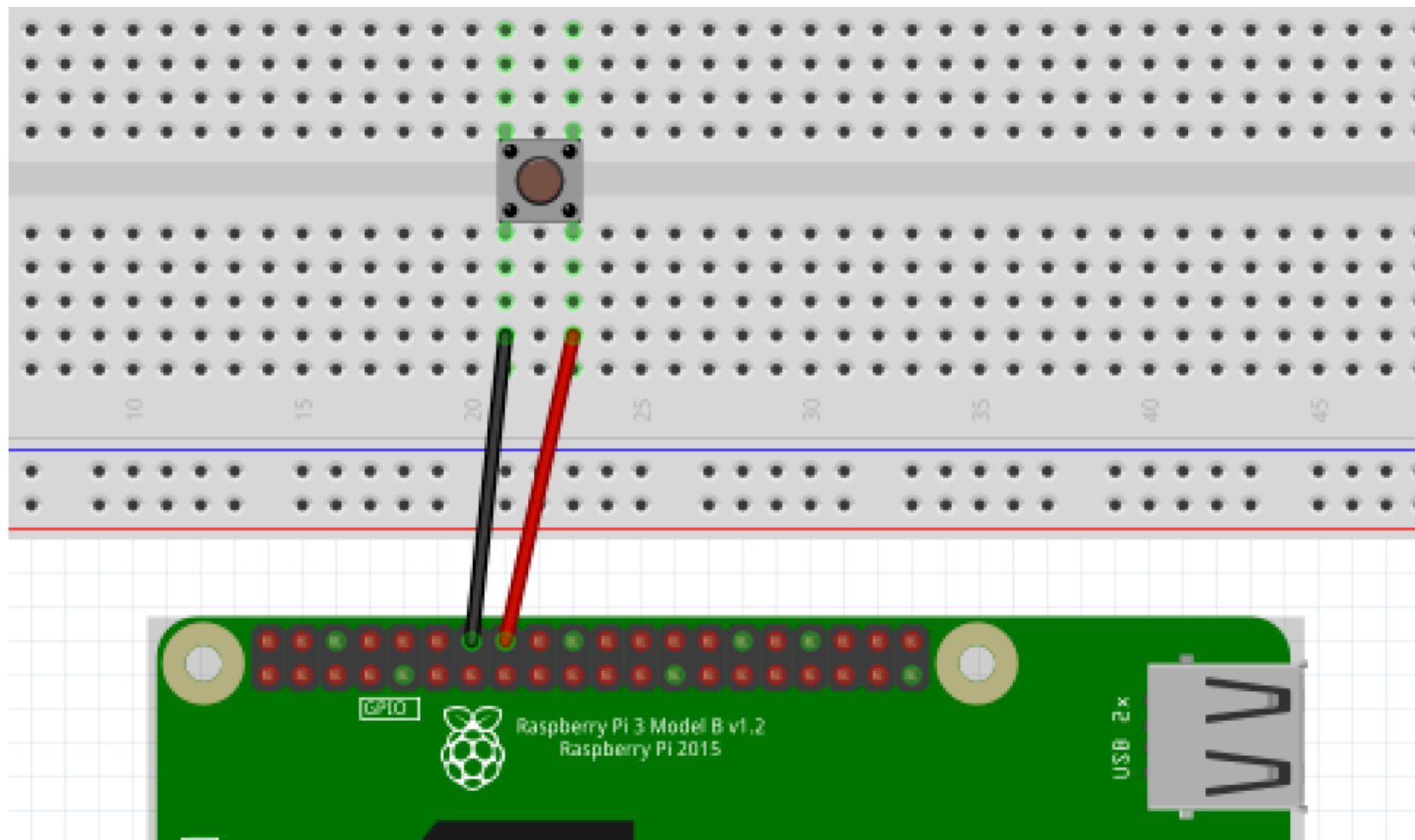

Pin#	GPIO#	Connection
------	-------	------------

14	GND	Button pin
----	-----	------------

16	GPIO23	Button pin
----	--------	------------


# Using a button to control an LED

## **Additional parts needed**

- LED
- 330  $\Omega$  resistor
- Push button switch
- Connecting wires
  - 4 Male-Female wires



# Using a button to control an LED


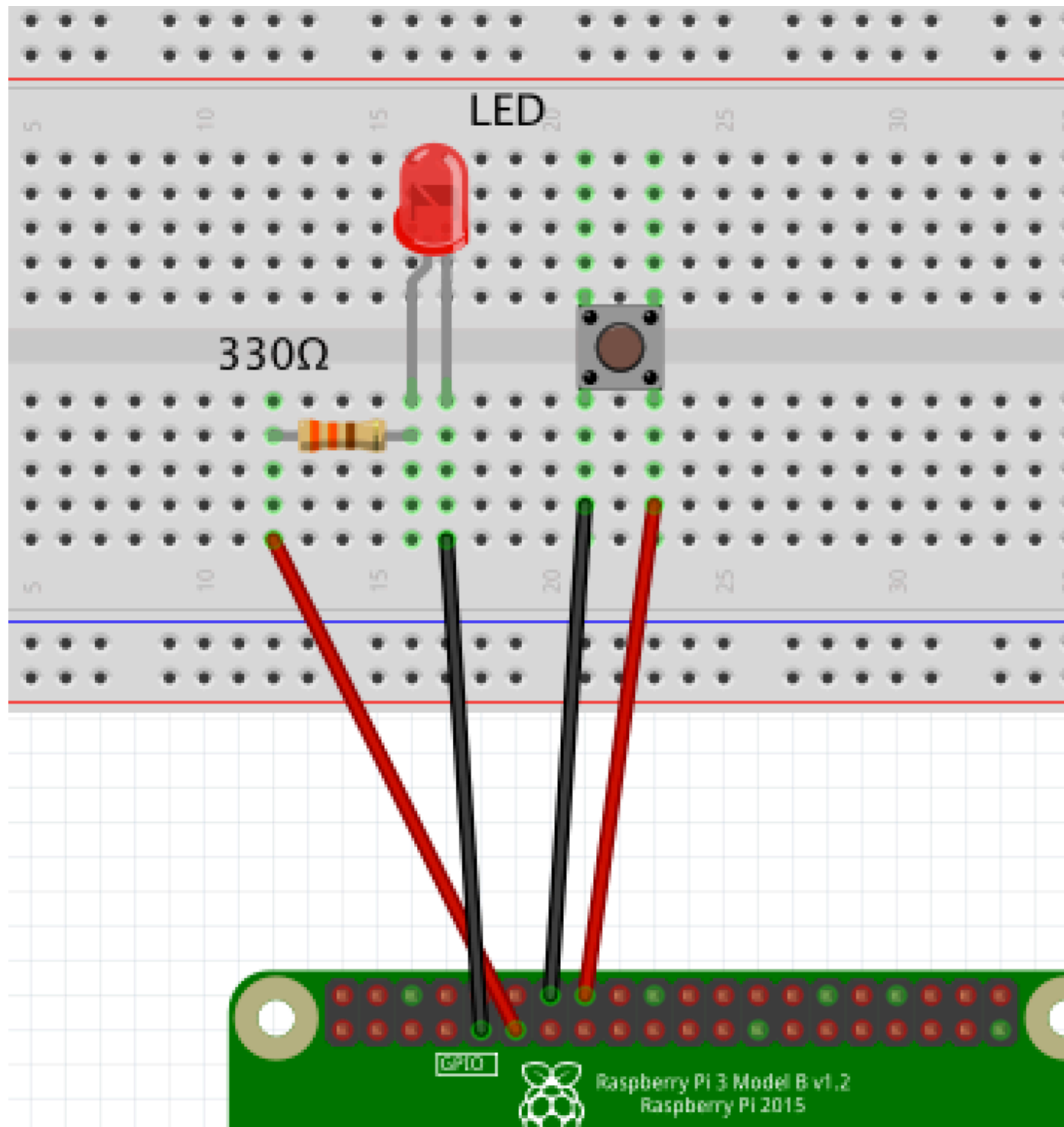


Pin#	GPIO#	Connection
14	GND	Button pin
16	GPIO23	Button pin
11	GPIO17	Resistor to LED Anode
9	GND	LED Cathode

# Working with a PIR Sensor

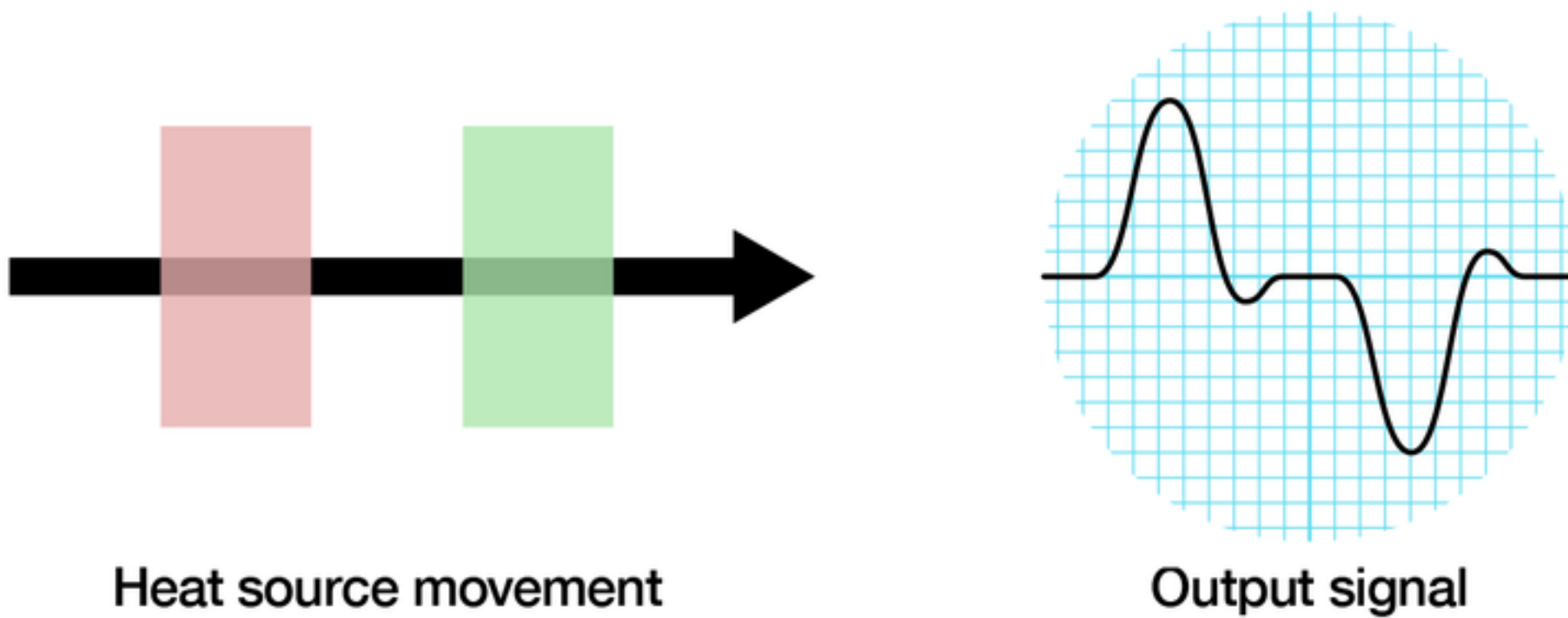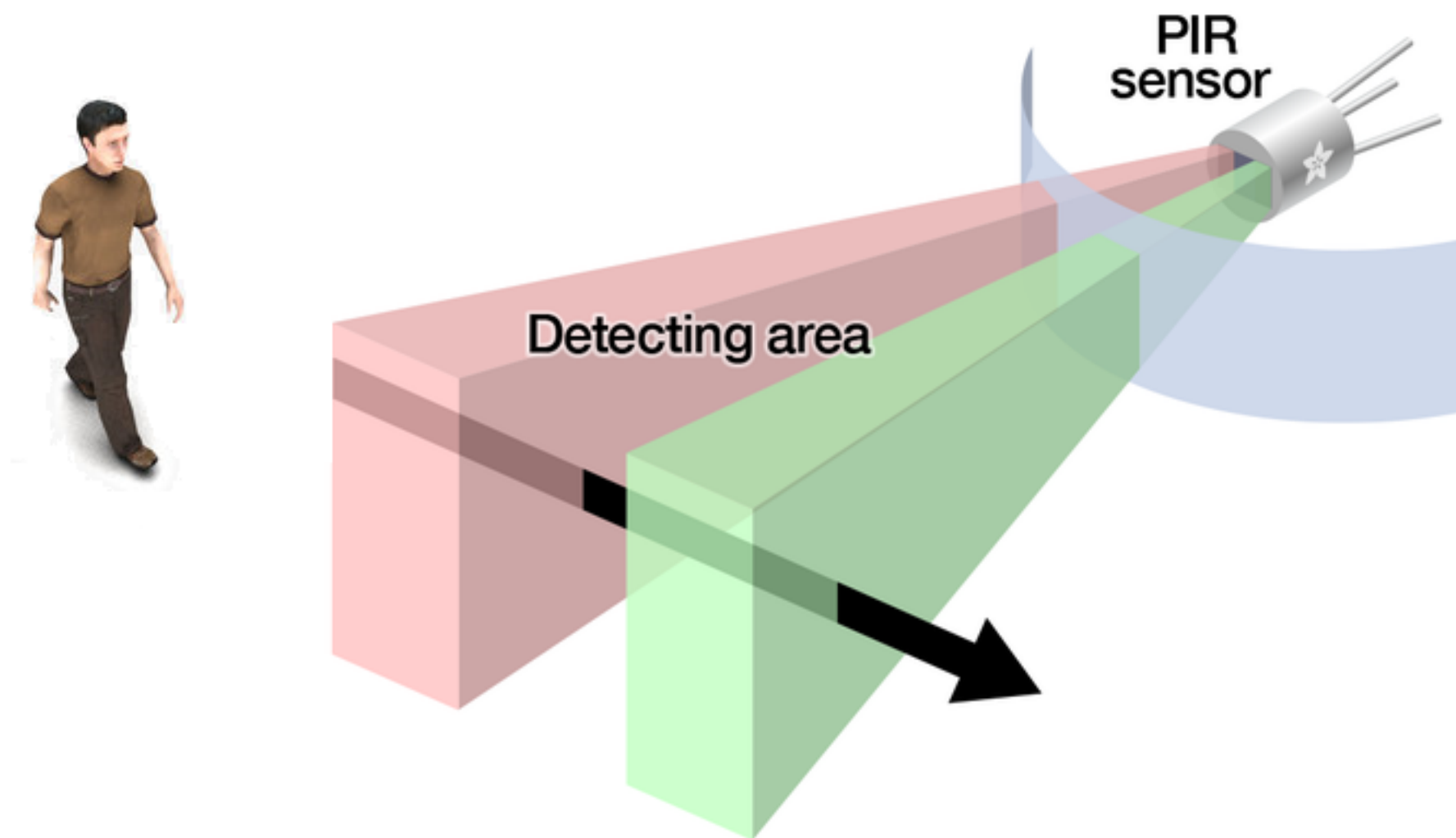
## **Additional parts needed**

- PIR Sensor
- Connecting wires
  - 3 Female-Female wires





# PIR sensor

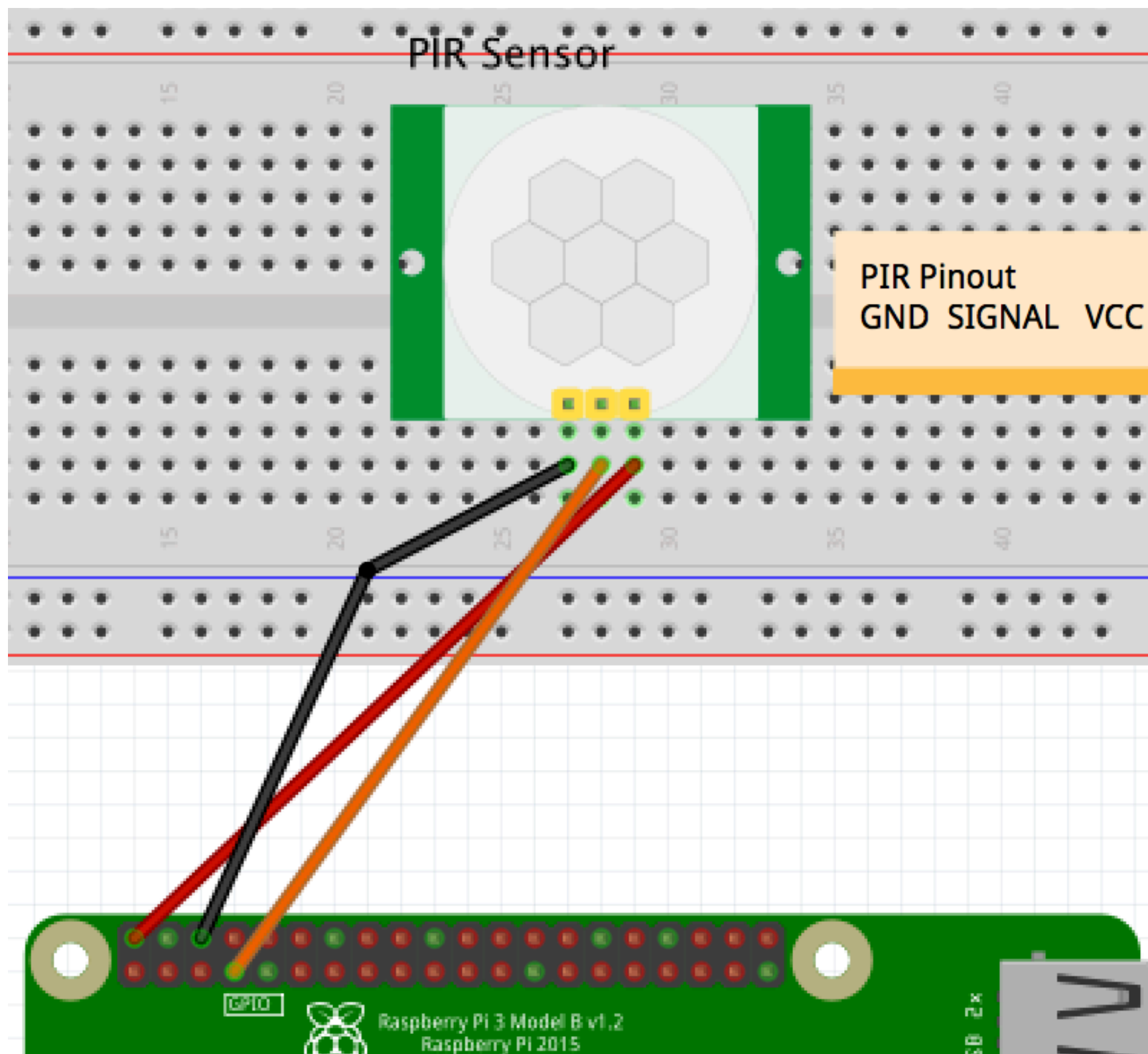


Pin#	GPIO#	Connection
2	5V	PIR - VCC
6	GND	PIR - GND
7	GPIO4	PIR - Signal

# PIR Sensor Alarm

## **Additional arts needed**

- PIR Sensor
- Piezo Buzzer
- 330  $\Omega$  resistor
- Connecting wires
  - 3 Female-Female wires
  - 2 Male-Female wires

# PIR sensor alarm

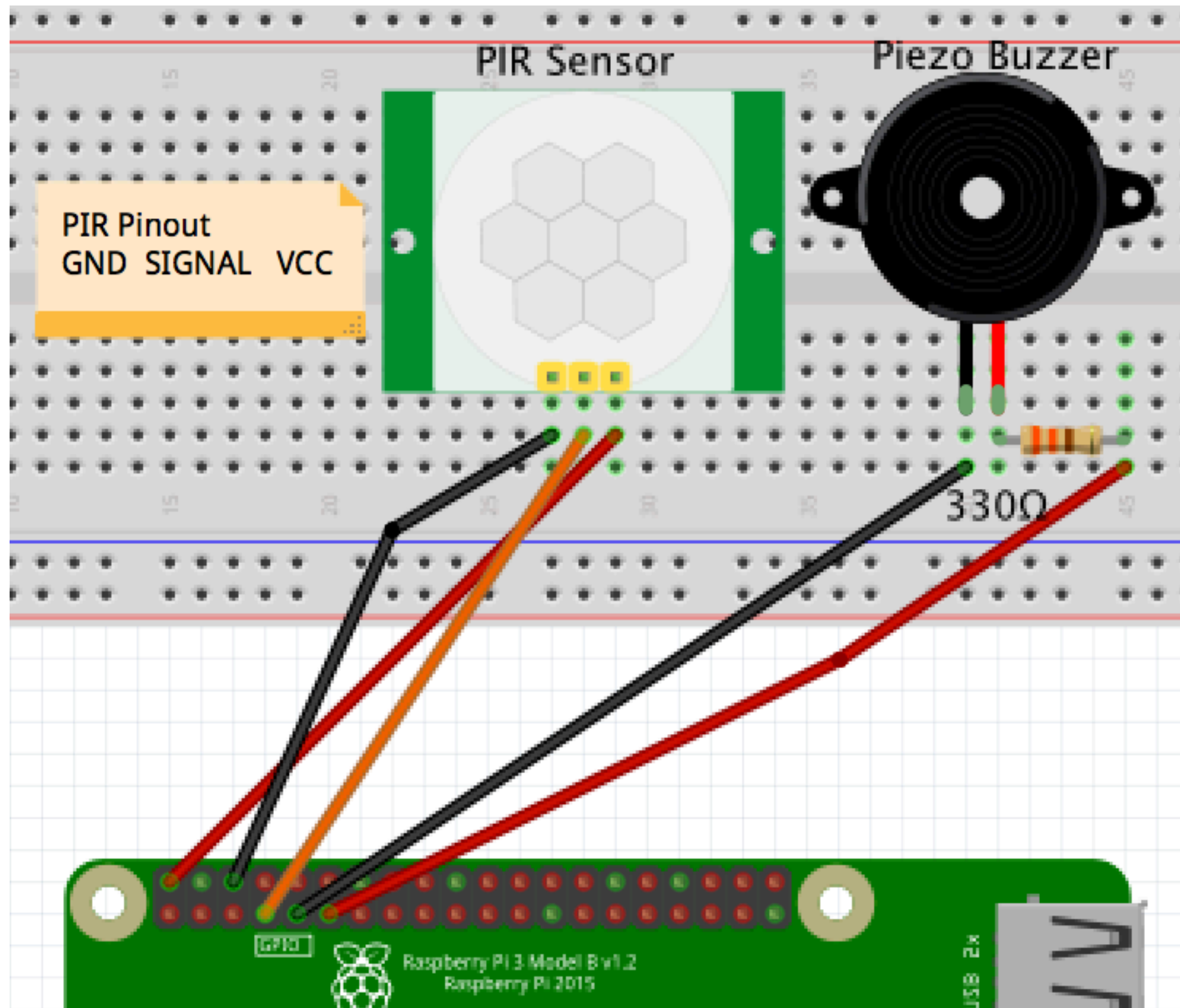

Pin#	GPIO#	Connection
2	5V	PIR - VCC
6	GND	PIR - GND
7	GPIO4	PIR - Signal
11	GPIO17	Resistor to +ve piezo
9	GND	-ve piezo