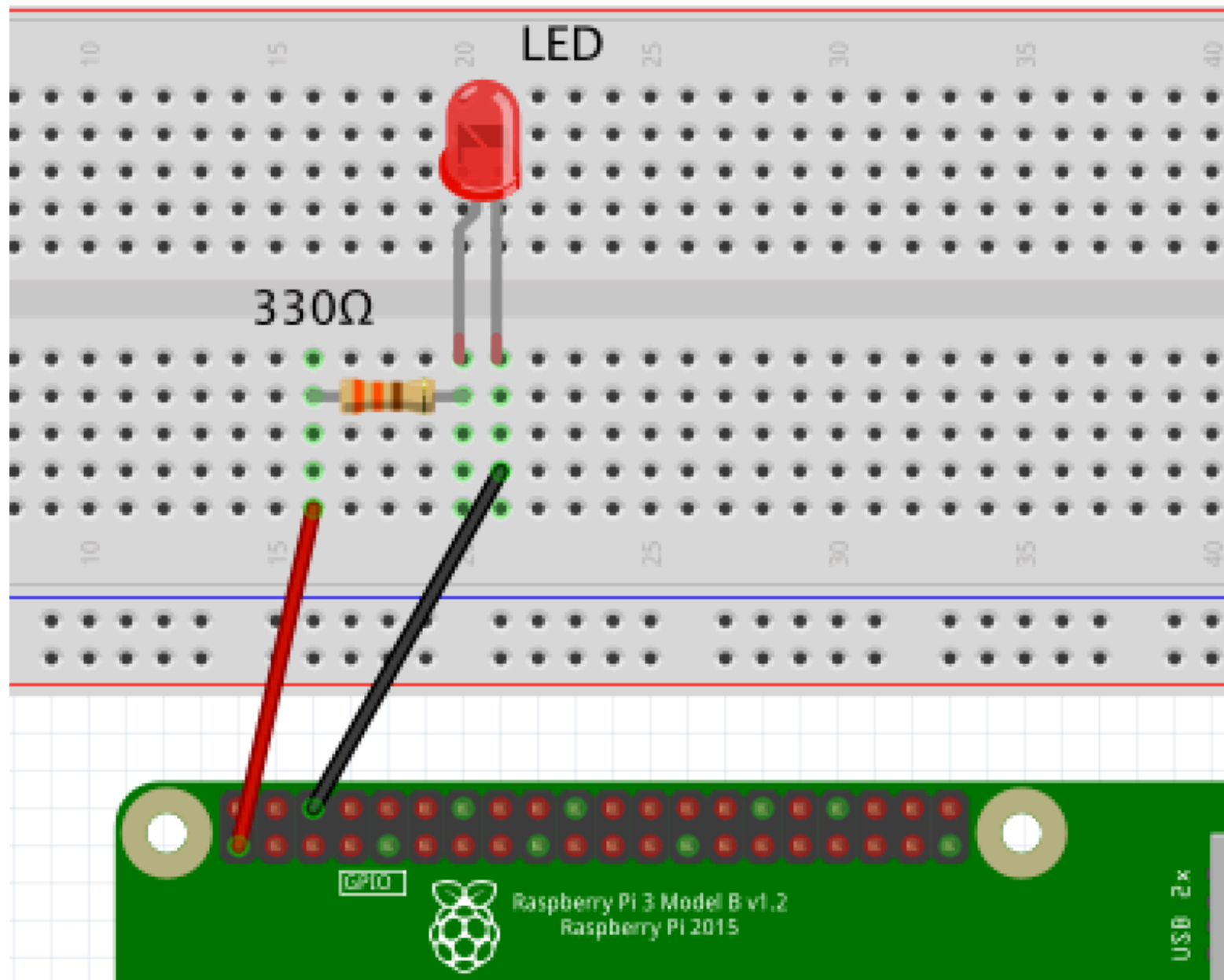


Power an LED

Additional parts needed

- LED
- 330 Ω resistor
- Connecting wires
 - 2 Male-Female wires

Power an LED



Pin#	GPIO#	Connection
1	3.3V	Resistor to LED Anode
6	GND	LED Cathode