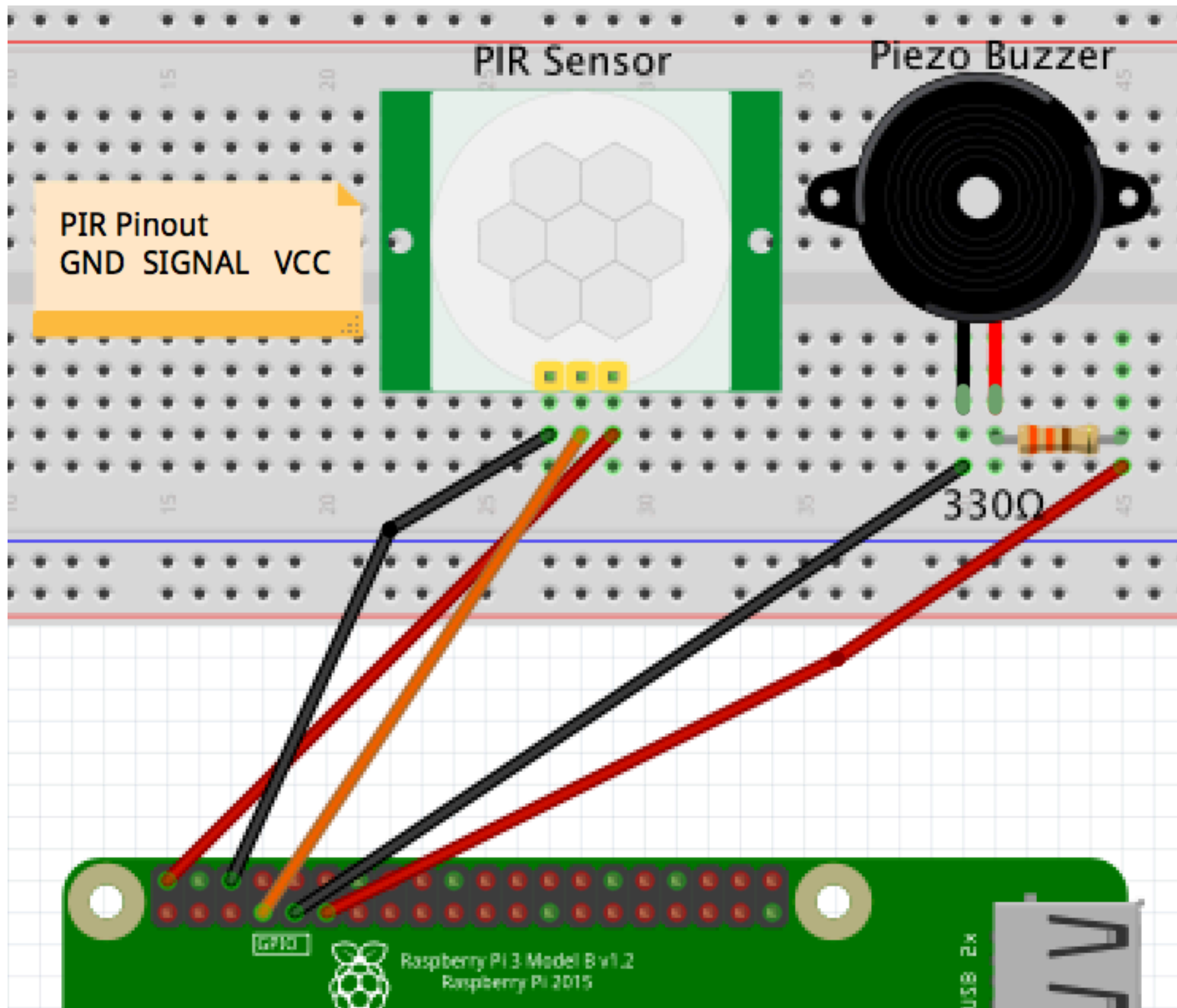


PIR Sensor Alarm

Additional arts needed

- PIR Sensor
- Piezo Buzzer
- 330 Ω resistor
- Connecting wires
 - 3 Female-Female wires
 - 2 Male-Female wires

PIR sensor alarm



Pin#	GPIO#	Connection
2	5V	PIR - VCC
6	GND	PIR - GND
7	GPIO4	PIR - Signal
11	GPIO17	Resistor to +ve piezo
9	GND	-ve piezo